

Part A.

Circuit in series

1. Total resistance in ohm

$$\begin{aligned}\text{Total resistance (R)} &= 20 + 30 + 50 \\ &= 100 \Omega\end{aligned}$$

2. Total current from power supply

$$I = V/R$$

$$V = 125$$

$$R = 100$$

$$\frac{125}{100} = 1.25 \text{ A}$$

3. Current through each resistor

Since it is series its the same

$$I_1 = 1.25 \text{ A}$$

$$I_2 = 1.25 \text{ A}$$

$$I_3 = 1.25 \text{ A}$$

4. Voltage drop across each resistor

$$V = IR$$

$$20 \Omega \text{ resistor} = 1.25 \times 20 = 25 \text{ V}$$

$$30 \Omega \text{ resistor} = 1.25 \times 30 = 37.5 \text{ V}$$

$$50 \Omega \text{ resistor} = 1.25 \times 50 = 62.5 \text{ V}$$

5. Power dissipated through each resistor

Watts law : Power = Voltage * Current

$$20 \Omega \text{ resistor} = 25 \times 1.25 = 31.25 \text{ W}$$

$$30 \Omega \text{ resistor} = 37.5 \times 1.25 = 46.875 \text{ W}$$

$$50 \Omega \text{ resistor} = 62.5 \times 1.25 = 78.125 \text{ W}$$

Circuit in parallel.

1. Total resistance

$$\frac{1}{R_T} = \frac{1}{20} + \frac{1}{100} + \frac{1}{50} = \frac{5+1+2}{100}$$
$$= \frac{8}{100}$$

$$\frac{1}{R_T} = 0.08$$

$$R_T = \text{inverse of } 0.08$$

$$= \frac{1}{0.08}$$

$$R_T = 12.5 \Omega$$

2. Total current from power supply

ohms law:

$$I = V/R = 126/12.5$$

$$I = 10A$$

3. Current through each resistor

in parallel voltage is same across:

$$20 \Omega \text{ resistor} = \frac{126}{20} = 6.25 A$$

$$100 \Omega \text{ resistor} = \frac{126}{100} = 1.26 A$$

$$50 \Omega \text{ resistor} = \frac{126}{50} = 2.5 A$$

4. Voltage drop across each resistor

$$V_1 = 126 V$$

$$V_2 = 126 V$$

$$V_3 = 126 V$$

5. Power dissipated through each resistor.

$$P = VI$$

$$20 \Omega \text{ resistor} : P = 126 \times 6.25 = 781.25 W$$

$$100 \Omega \text{ resistor} : P = 126 \times 1.25 = 156.25 W$$

$$50 \Omega \text{ resistor} : P = 126 \times 2.5 = 312.5 W$$